

# Electrical loading corrections

The sensitivity of a hydrophone is often specified as the end-of-cable open-circuit sensitivity. This is the sensitivity of the hydrophone at the end of its cable when not connected to an electrical load. When a specific electrical load, such as an oscilloscope, an amplifier or extra cable is used at the output of the hydrophone, the end-of-cable loaded sensitivity of the hydrophone may be related to the open-circuit sensitivity in the following way.

## Corrections using complex impedance

Consider the general case in which the hydrophone is considered as a two-terminal network of complex impedance  $Z_H$  connected to an electrical load of complex impedance  $Z_L$ . The end-of-cable loaded sensitivity of the hydrophone,  $M_L$ , when connected to the specified load is related to the end-of-cable open-circuit sensitivity,  $M_O$ , by

$$M_L = M_O \sqrt{\frac{\operatorname{Re}(Z_L)^2 + \operatorname{Im}(Z_L)^2}{[\operatorname{Re}(Z_L) + \operatorname{Re}(Z_H)]^2 + [\operatorname{Im}(Z_L) + \operatorname{Im}(Z_H)]^2}}$$

where Re and Im denote the real and imaginary parts of the relevant complex impedance.

Often, the electrical load can be assumed to be a parallel combination of a resistance  $R_L$  and capacitance  $C_L$ . In this case,  $\operatorname{Re}(Z_L)$  and  $\operatorname{Im}(Z_L)$  are given by

$$\operatorname{Re}(Z_L) = \frac{R_L}{1 + \omega^2 C_L^2 R_L^2}$$

and

$$\operatorname{Im}(Z_L) = \frac{-\omega C_L R_L^2}{1 + \omega^2 C_L^2 R_L^2}$$

where  $\omega$  is the angular frequency.

## Corrections using only capacitance values

A further simplification is possible if the impedances of both the hydrophone and the load can be assumed to be purely capacitive. This is often a valid assumption for a hydrophone at frequencies much less than the resonance frequency and for loads such as extension cables. In this case, if  $C_H$  is the end-of-cable capacitance of the hydrophone *including* any integral cable and connector, the above equation reduces to:

$$M_L = M_o \left[ \begin{array}{c} C_H \\ C_H + C_L \end{array} \right] \quad (1)$$

---

***For further information, contact:***

Stephen Robinson  
Centre for Mechanical and Acoustical Metrology  
National Physical Laboratory  
Hampton Road  
Teddington  
Middlesex TW11 0LW  
United Kingdom  
Tel: 020 8943 7152  
Fax: 020 8943 6217  
Email: [stephen.robinson@npl.co.uk](mailto:stephen.robinson@npl.co.uk)

Or, why not visit the NPL Acoustics web pages at: <http://www.npl.co.uk/acoustics>